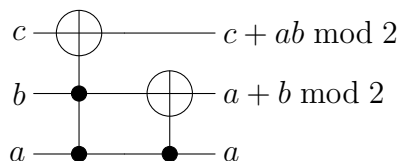


Challenge Problem 2
 CPSC 489/689 Quantum Algorithms
 Andreas Klappenecker

The following quantum circuit represents a half-adder; it calculates the sum $a + b \bmod 2$, and the carry ab of the inputs a and b :



The circuit implements a unitary matrix U_{add} , which is determined by

$$\begin{aligned}
 U_{add}|000\rangle &= |000\rangle, & U_{add}|100\rangle &= |100\rangle, \\
 U_{add}|001\rangle &= |011\rangle, & U_{add}|101\rangle &= |111\rangle, \\
 U_{add}|010\rangle &= |010\rangle, & U_{add}|110\rangle &= |110\rangle, \\
 U_{add}|011\rangle &= |101\rangle, & U_{add}|111\rangle &= |001\rangle.
 \end{aligned}$$

Let $m(U)$ denote the minimal number of controlled-not and single qubit gates, which are needed to realize $U \in \mathcal{U}(2^n)$. The challenge is to determine $m(U_{add})$. In other words, how many controlled-not gates and single qubits gates are needed in an optimal implementation of U_{add} ? You need to prove your result.

Remark. Let T denote the unitary matrix corresponding to the Toffoli gate. Notice that $|m(T) - m(U_{add})| \leq 1$.

I offer a **Challenges in Quantum Computing Award**, worth US\$ 100, for the first correct solution to this problem.

Andreas Klappenecker